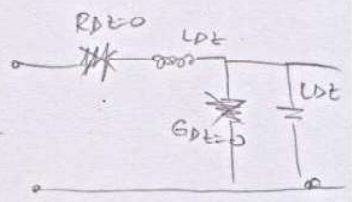


in LOSSLESS LINE many cases, the loss of the line is very small:

(6)

$$R = G = 0$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$



$$\gamma = \alpha + j\beta = j\omega \sqrt{LC}$$

$$\beta = \omega \sqrt{LC} \quad (2.12.a)$$

$$\alpha = 0 \quad (2.12.b)$$

↳ for a lossless line the attenuation constant is zero.

The characteristic impedance is $Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$

$$Z_0 = \sqrt{\frac{L}{C}} \quad (2.13) \rightarrow \text{Real Number.}$$

→ General solution for voltage and current on a lossless line

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} \quad (2.14a)$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z} \quad (2.14b)$$

wavelength :

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{LC}} \quad (2.15)$$

$$v_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$v_p = \frac{1}{\sqrt{LC}} \quad (2.16)$$